

A breadboard is a tool used to temporarily connect electronic components together. It has a grid of holes that allow you to easily insert and connect wires and components.

What it looks like:

- A breadboard is a rectangular board with a grid of holes.
- The holes are connected in rows and columns.
- There are usually two long, continuous rows of holes on the sides for power supply.

How it works:

- **Power Rails:** The long rows on the sides are called power rails. One is typically connected to positive voltage (like 5V), and the other is connected to ground (0V).
- **Component Insertion:** You insert the legs of electronic components (like resistors, LEDs, and transistors) into the holes.
- **Connecting Components:** The holes in each row are electrically connected, allowing you to easily connect components together using jumper wires.

Using a Breadboard:

1. **Find the Power Rails:** Identify the power rails on the breadboard.
2. **Insert Components:** Insert the legs of your components into the holes. Make sure the legs are inserted far enough so they make good contact.
3. **Connect Components:** Use jumper wires to connect the components together according to your circuit diagram.
4. **Apply Power:** Connect the power supply to the power rails.

Why use a breadboard?

- **Easy to Use:** Breadboards are easy to use and don't require any soldering.
- **Reusable:** You can easily remove components and rearrange them to try different circuits.
- **Great for Learning:** Breadboards are a great way to learn about electronics and how circuits work.

Let's build a simple circuit!

Imagine you want to make a simple circuit with an LED. Here's how you would do it on a breadboard:

1. **Find the Power Rails:** Identify the positive and negative power rails on the breadboard.
2. **Insert the LED:** Insert the longer leg (anode) of the LED into a hole connected to the positive power rail. Insert the shorter leg (cathode) into a hole in a different row.
3. **Add a Resistor:** Insert a resistor into the same row as the LED's cathode.
4. **Connect the Resistor:** Connect the other end of the resistor to a hole connected to the negative power rail.

[How to Use a Breadboard \(with Example\)](#)

