

The magic of the 74HC595 shift register lies in how it controls each LED individually while still using only a few pins from the microcontroller.

## How Can One 5V Input Control All LEDs?

The 74HC595 shift register **does not directly send the same 5V to all LEDs at once**. Instead:

1. It acts like a **switch** for each LED.
2. Each LED is connected to a separate output pin of the shift register.
3. The shift register switches each output pin **on or off** (HIGH or LOW) based on the binary data you shift into it.

This is achieved through the **current-sourcing and sinking capability** of the shift register. Here's what happens:

- When an output pin is HIGH, it provides 5V to the LED.
- When an output pin is LOW, it acts as a ground connection (0V).

## Why Doesn't Voltage Drop When Multiple LEDs Are On?

The answer lies in **Ohm's Law**, proper circuit design, and how current flows:

1. **Voltage Is Constant Across Parallel Connections:**
  - Each LED is connected to its own output pin of the shift register.
  - These connections are effectively **parallel** from the perspective of the power supply.
  - In a parallel circuit, the voltage (5V) stays the same across all branches.
  - This means every LED sees the full 5V (or whatever is supplied to the shift register).
2. **Current Is Divided, Not Voltage:**
  - The shift register manages the current flowing through each pin separately.
  - Each LED draws only the current it needs (usually a few milliamps, limited by a resistor).
  - The power supply needs to provide enough current to drive all LEDs simultaneously, but the voltage remains constant.
3. **Resistors Prevent Overcurrent:**
  - Each LED is typically connected in series with a resistor.
  - These resistors ensure that the current through each LED is limited, preventing them from drawing more than they need and protecting the shift register from overload.

## Key Takeaways

1. **5V Is Shared, But Current Is Divided:**
  - The 74HC595 doesn't "run out of voltage" because voltage is constant in a parallel circuit.
  - Instead, the power supply needs to handle the total current drawn by all LEDs (sum of currents through each branch).
2. **Each Output Pin Works Independently:**
  - The shift register can individually control the state (ON or OFF) of each pin, allowing fine-grained control over which LEDs are lit.
3. **The Role of Resistors:**
  - Each LED has its own resistor, ensuring proper current flow and preventing issues like brightness variations or damage.

## Why Shift Registers Are Efficient

In your previous setup, each LED had its own microcontroller pin. This works but is **not scalable** when you need to control many LEDs. A shift register reduces the number of microcontroller pins needed (just 3 pins in your case) while allowing control of multiple outputs, making it much more efficient.

[Maximum current from the 5V pin?](#)