

Electronic components, including **Arduino sensors and modules**, are designed to draw **only the amount of current they need** based on their internal circuitry and resistance.

How Sensors and Electronics Draw Current

1. Voltage is Supplied

- The Arduino or power supply provides a **fixed voltage** (e.g., 5V or 3.3V).
- The sensor or electronic component **determines how much current it needs** based on its internal resistance and circuit design.

2. Ohm's Law Applies

- The current drawn depends on **Ohm's Law**:

$$I = \frac{V}{R}$$

- If a component has a built-in resistor or internal circuit, it **limits the amount of current it takes**.

3. Components Only Take What They Need

- Unlike a **short circuit**, where current flows unrestricted, sensors and modules have a **designed operating range**.
- For example:
 - An **LED with a 220Ω resistor** at **5V** will draw about

$$I = \frac{5V}{220\Omega} = 22.7 \text{ mA}$$

- An **MG811 CO₂ sensor** has an **internal heating element** that draws around **200mA** when powered.

4. Arduino Digital Pins Have a Limit

- Arduino **pins do not "push" current**. Instead, **the connected device pulls only what it needs**.
- Each **digital pin** can provide **up to 20mA safely**, with a **max total of 200mA for all pins combined**.

What Happens If a Sensor Needs More Current?

If a sensor or module **requires more current than an Arduino pin can provide**, you need to:

- **Use an external power source (like a separate 5V supply)**
- **Use a transistor or MOSFET as a switch** to control high-current loads
- **Check the datasheet** to ensure the sensor is within safe limits

If you connect a sensor or any device that **draws more current than the Arduino pin can safely provide**, it can **damage or even permanently burn out the pin or the microcontroller itself**.

Why Can a High-Current Sensor Burn the Pin?

1. **Arduino Digital Pins Have a Current Limit**
 - Most Arduino boards (like the **Uno**) have a **maximum safe current per pin of 20mA** (absolute max **40mA**, but exceeding 20mA is risky).
 - The **total** current for all pins combined should not exceed **200mA**.
2. **Excess Current Can Overheat and Damage the Pin**
 - If a sensor **draws more current than the pin can handle**, the **pin's internal transistor (MOSFET) overheats**, potentially **burning out the pin permanently**.
 - Once burned out, the pin **may stop working completely** or behave unpredictably.
3. **Microcontroller Damage**
 - If a component **draws too much current**, it can also **damage the entire microcontroller (ATmega328P on an Uno)**, making the **Arduino unusable**.

Example: When a Sensor Draws Too Much Current

Bad Example: Connecting a 100mA sensor **directly to an Arduino pin**

- The pin may **overheat and get damaged**
- The sensor might not work properly

Good Example: Using a transistor to switch **external power**

- **Arduino controls the transistor**
- **Sensor gets full required current from an external power supply**

Key Takeaways

Sensors and electronic components **only draw the current they need**.

Arduino **provides voltage**, and the **component regulates its own current**.

High-current devices may need **external power** instead of drawing directly from the Arduino.

[Voltage, Current, Resistance, and Ohm's Law](#)