

Does a Copper Wire Have Resistance?

Yes, **copper wire** does have resistance. Although copper is an excellent conductor, it is not perfect. The resistance of a copper wire depends on:

1. **Length**: Longer wires have more resistance.
2. **Cross-sectional area (thickness)**: Thicker wires have less resistance.
3. **Temperature**: Higher temperatures increase resistance.

The resistance RRR of a copper wire can be calculated using the formula:

$$R = \rho * L / A$$

Where:

- ρ is the resistivity of copper ($1.68 \times 10^{-8} \Omega \text{ m}$ at 20°C),
- L is the length of the wire in meters,
- A is the cross-sectional area in square meters.

For most household wiring, this resistance is very small but not zero.

Imaginary Wire with Zero Resistance

If you have an **ideal wire with zero resistance**, then the current (I) in the wire depends only on the **voltage** (V) and the **load resistance** connected to it (if any). Ohm's Law applies:

$$I = V / R$$

Where:

- V is the voltage (120V in this case),
- R is the total resistance in the circuit.

What Happens with R=0R?

If the resistance is **0 ohms**, the formula becomes:

$$I = 120 / 0$$

This results in a **mathematical infinity**. In practical terms:

- If there is no resistance to limit the current, the current can theoretically become infinite.
- In reality, this would cause the wire to draw as much current as the power source can supply.

Real-World Constraints

In practice:

1. Power sources (like a household outlet or power plant) have **maximum current limits** based on their design.
 - A typical household outlet is limited to **15-20 amps** due to circuit breakers.
 - Even power plants cannot supply infinite current; they have physical and engineering constraints.
2. If an ideal zero-resistance wire were connected to a power source, it would result in a **short circuit**, likely tripping the circuit breaker or damaging the source.

Summary

1. Copper wires have a small but nonzero resistance.
2. For a wire with **0 resistance**:
 - Theoretically, it could carry an infinite current at a fixed voltage.
 - In practice, the current would be limited by the power source's maximum capacity, and a short circuit would occur.
3. Zero-resistance wires don't exist in reality, but **superconductors** (materials with no resistance at very low temperatures) are the closest equivalent. Even then, practical current limits depend on the power supply and other factors.

[Resistance](#)

[How to Test for Resistance? What is Continuity?](#)