

What is ULN2003?

The **ULN2003** is a **high-voltage, high-current Darlington transistor array IC**. It is commonly used as a driver for controlling loads such as stepper motors, relays, and LEDs. It contains **seven Darlington transistor pairs** (hence "array"), which allow it to switch and control high-current and high-voltage devices using low-power control signals from microcontrollers or logic circuits.

How ULN2003 Works

1. Internal Structure:

- The ULN2003 has **seven Darlington pairs**, each consisting of two transistors connected in such a way to provide high current gain. This means a small input current on the base of the first transistor can control a large output current.
- Each input pin corresponds to an output pin, allowing the IC to control up to **7 separate devices**.
- It also includes **flyback diodes** to protect against voltage spikes generated by inductive loads (e.g., motors, relays).

2. Pin Configuration:

- **Pins 1–7 (Inputs)**: Receive signals from the microcontroller or logic circuit.
- **Pins 10–16 (Outputs)**: Drive the connected loads, such as motor windings or relays.
- **Pin 8 (GND)**: Ground pin for the IC.
- **Pin 9 (COM)**: Common pin connected to the power source of the inductive loads, used for flyback protection.

3. Operating Principle:

- When a HIGH signal is applied to an input pin, the corresponding Darlington pair is activated, allowing current to flow from the output pin to ground. This completes the circuit for the load connected to the output pin.
- If the input pin is LOW, the Darlington pair remains off, and no current flows through the output pin.

Key Features of ULN2003

- **Voltage Support:** Can handle loads up to **50V**.
- **Current Support:** Each channel can sink up to **500mA** of current.
- **Flyback Diodes:** Built-in protection for inductive loads to prevent damage from back EMF.
- **Ease of Use:** Simple to interface with microcontrollers like Arduino, Raspberry Pi, etc.

Applications

1. **Stepper Motors:**
 - Often used with stepper motors like the **28BYJ-48**. The ULN2003 can drive the four coils of the stepper motor, with the microcontroller providing the control signals.
2. **Relays:**
 - Controls high-power devices through relays by providing the required current to energize the relay coil.
3. **LED Arrays:**
 - Drives multiple high-power LEDs or LED arrays where higher currents are needed.
4. **Solenoids:**
 - Controls solenoid-based actuators in automation projects.

Advantages of ULN2003

1. **High Current Gain:**
 - The Darlington pair configuration amplifies the input signal, allowing it to drive high-current loads with low-power microcontroller outputs.
2. **Flyback Diode Protection:**
 - Makes it ideal for driving inductive loads, ensuring longevity and reliability of connected components.
3. **Compact Design:**
 - Drives multiple loads in a single IC, saving space on the circuit board.
4. **Ease of Interfacing:**
 - Compatible with TTL and CMOS logic levels, making it straightforward to connect to microcontrollers.

Why Not Use Regular Transistors?

The ULN2003 simplifies the design by integrating:

- Multiple transistors.
- Flyback diodes.
- A shared ground and compact form factor. This reduces the component count and wiring complexity compared to using individual transistors and diodes.

The **VCC** for the load and the control voltage from the microcontroller can operate independently, making the ULN2003 versatile and compatible with various systems.

[What is ULN2003 IC | How UNL2003 IC Works](#)